

Introduction to VHDL




Modules #6 and #7

Digilent Inc. Course

Data Selectors / Multiplexers



S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

4:1 mux truth table

 

Mux circuit symbol

Bus Multiplexer

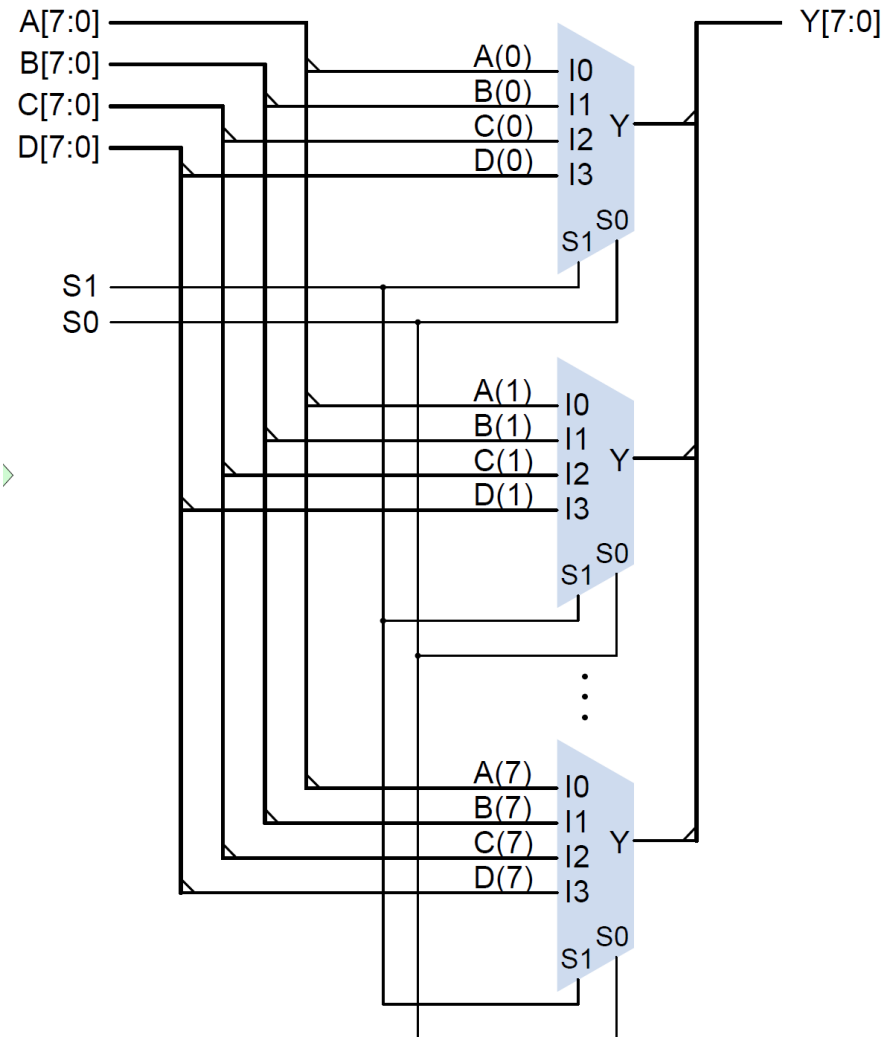 

MUX VHDL Example:

Selected Signal Assignment

```
entity mux_select is  
  port ( I3, I2, I1, I0: in std_logic;  
         sel  : in std_logic_vector (1 downto 0);  
         Y    : out std_logic);  
end mux_select;
```

```
architecture behavioral of mux_select is  
Begin  
  with sel select  
    Y <= I0 when "00";  
        I1 when "01";  
        I2 when "10";  
        I3 when "others";  
end behavioral;
```

Bus MUX VHDL Example: Selected Signal Assignment

```
entity busmux_select is  
  port ( I3, I2, I1, I0: in std_logic_vector (7 downto 0);  
         sel      : in std_logic_vector (1 downto 0);  
         Y        : out std_logic_vector (7 downto 0));  
end busmux_select;
```


```
architecture behavioral of busmux_select is  
Begin  
  with sel select  
    Y <= I0 when "00";  
        I1 when "01";  
        I2 when "10";  
        I3 when "others";  
end behavioral;
```

More Complex MUX VHDL: Conditional Assignment

```
entity mux_cond is  
  port ( A, B, C : in std_logic_vector (7 downto 0);  
         Sel      : in std_logic_vector (1 downto 0);  
         Y        : outstd_logic_vector (7 downto 0));  
end mux_cond;
```

```
architecture behavioral of mux_cond is  
Begin  
  Y <= (A or not C) when (Sel = "00") else  
        (A xor B) when (Sel = "01") else  
        not A when (Sel = "10") else  
        (B nand C);  
end behavioral;
```

Decoder

 


**3:8 binary
decoder**

Decoder VHDL Example: Selected Signal Assignment

```
entity decoder is  
  port ( in:      in std_logic_vector (1 downto 0);  
         Y:       out std_logic_vector (7 downto 0));  
end decoder;
```

```
architecture behavioral of decoder is  
Begin  
  with in select  
  Y <=  "0001" when "00";  
        "0010" when "01";  
        "0100" when "10";  
        "1000" when "others";  
end behavioral;
```



DeMultiplexer (DeMUX)

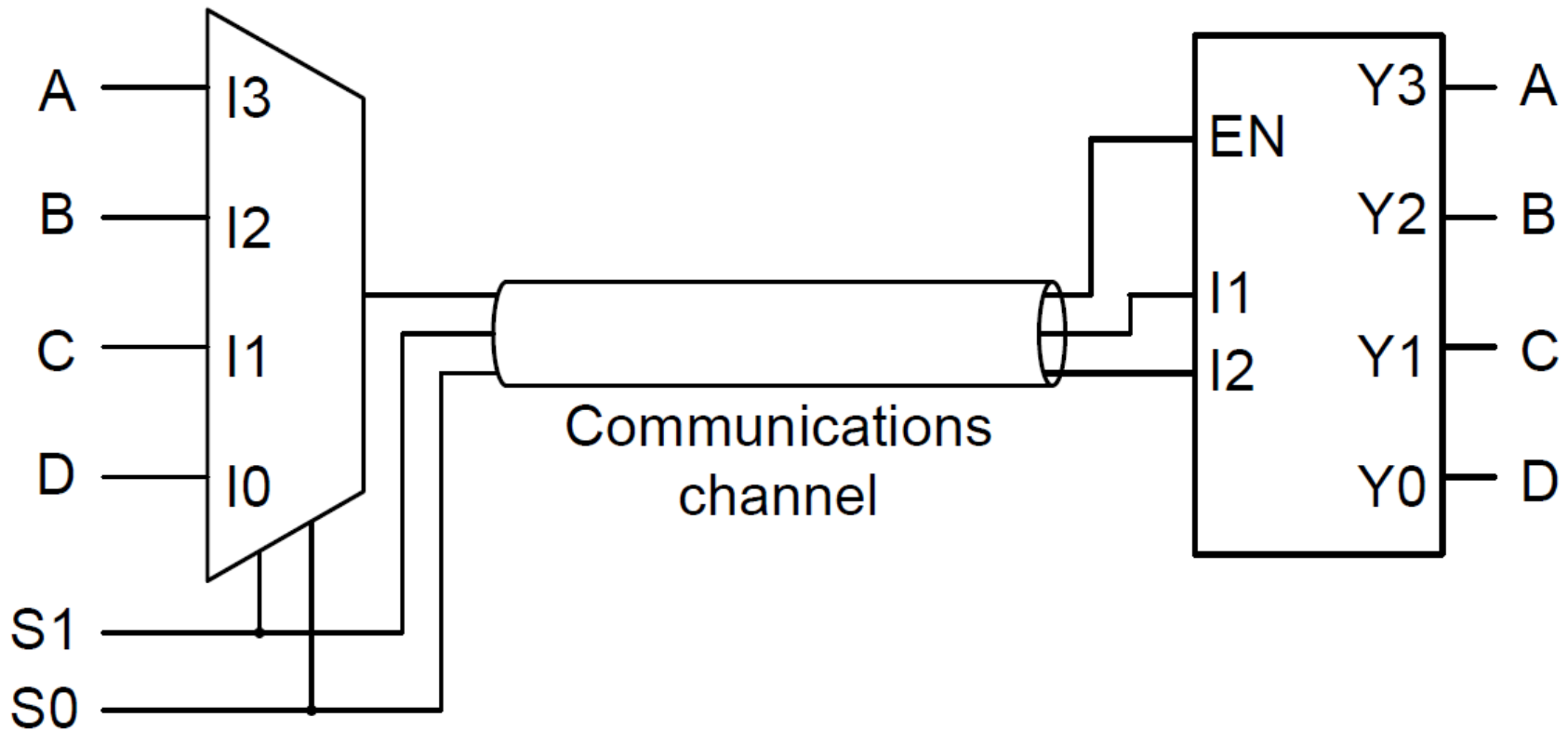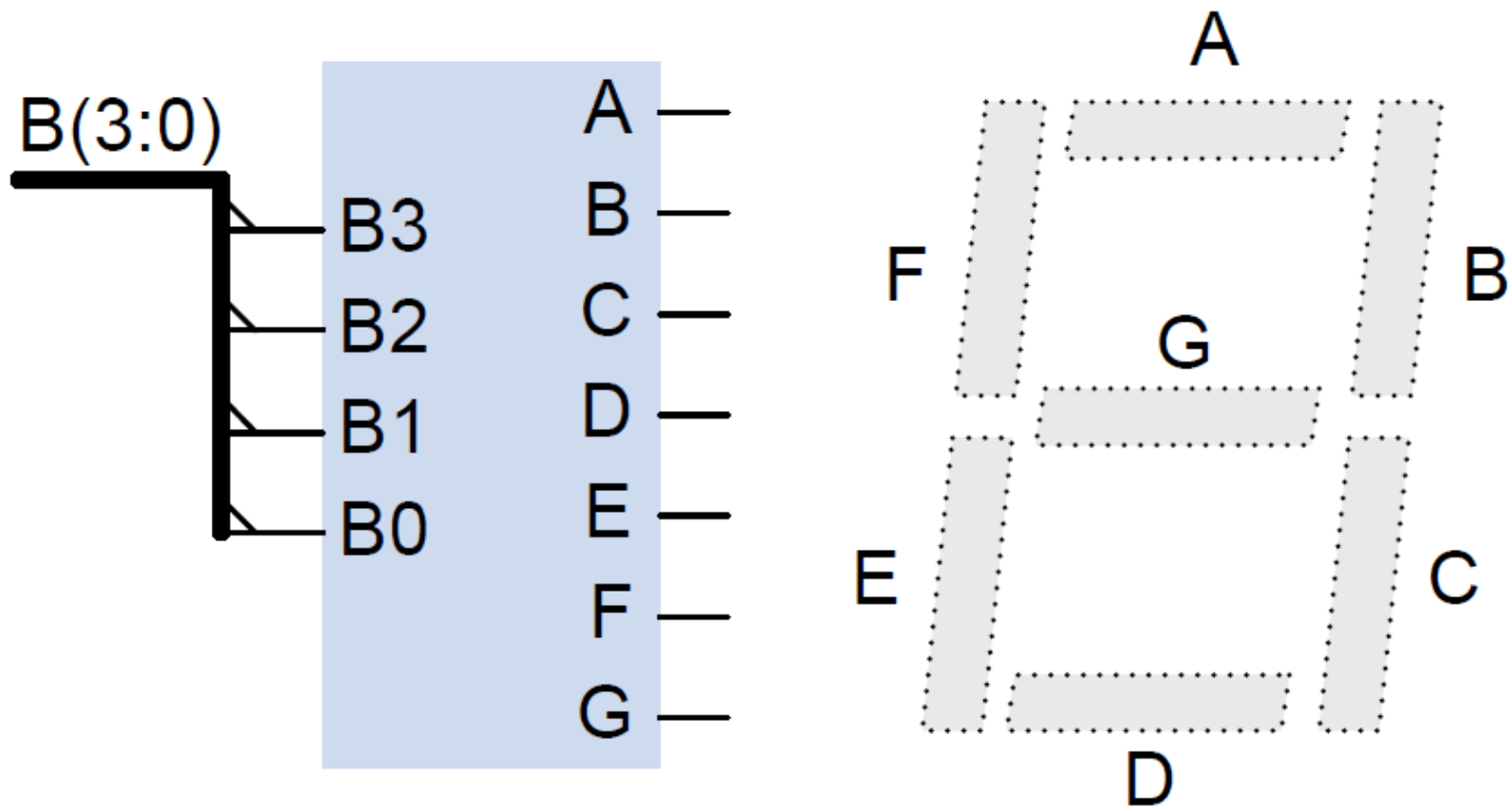

DeMUX VHDL Code

- Assignment: modify the code of a MUX to implement a DeMUX

7-Segment Decoder




7-Segment Decoder VHDL Code

```
entity seven_seg_dec is  
    port (bin: in STD_LOGIC_VECTOR (3 downto 0);  
          segout : out STD_LOGIC_VECTOR (6 downto 0));  
end seven_seg_dec;
```

```
architecture behavioral of seven_seg_dec is  
begin  
    with bin select  
        segout <= "1111110" when "0000";  
                "0110000" when "0001";  
                .  
                .  
                "0000001" when others;  
end behavioral;
```

Priority Encoder

 

**Priority
Encoder**

entity encoder **is**

port (ein :

I :

eout, gs :

Y :

end encoder;

in std_logic;

in std_logic_vector (3 **downto** 0);

out std_logic;

out std_logic_vector (1 **downto** 0));

architecture Behavioral **of** encoder **is**

Begin

eout <= ein **and not** I(3) **and not** I(2) **and not** I(1) **and not** I(0);







gs <= ein **and** (I(3) **or** I(2) **or** I(1) **or** I(0));

Y(1) <= I(3) **or** I(2);

Y(0) <= I(3) **or** I(1);

end Behavioral;

Shifters

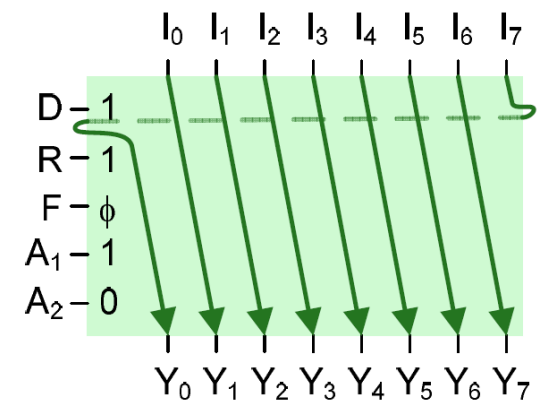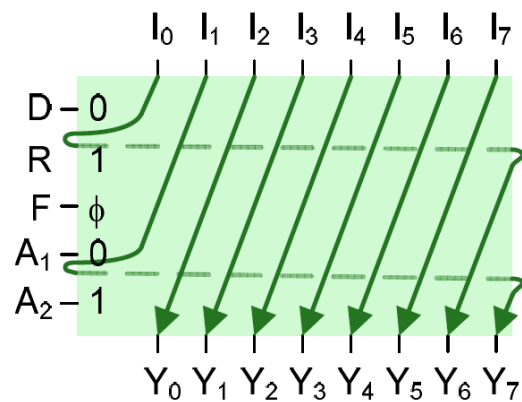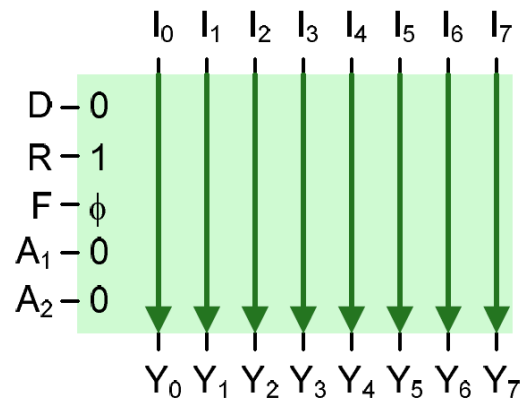   

Shifters

EN	R	D	Y ₃	Y ₂	Y ₁	Y ₀
0	ϕ	ϕ	0	0	0	0
1	0	0	I ₂	I ₁	I ₀	0
1	0	1	0	I ₃	I ₂	I ₁
1	1	0	I ₂	I ₁	I ₀	I ₃
1	1	1	I ₀	I ₃	I ₂	I ₁

Truth table for 4-bit shifter with shift/rotate left/right functions


Shifters VHDL Example

```
entity my_shift is  
  port ( din:      in std_logic_vector (7 downto 0);  
         r, d, en: in std_logic;  
         dout:     out std_logic_vector (7 downto 0));  
end my_shift;
```


```
architecture my_shift_arch of my_shift is  
begin  
  dout <= "00000000" when en = '0' else  
    din(6 downto 0) & din(7) when (r = '1' and d = '0') else  
    din(0) & din(7 downto 1) when (r = '1' and d = '1') else  
    din(6 downto 0) & '0' when (r = '0' and d = '0') else  
    '0' & din(7 downto 1);  
end my_shift_arch;
```


Bit-Slice Design Method

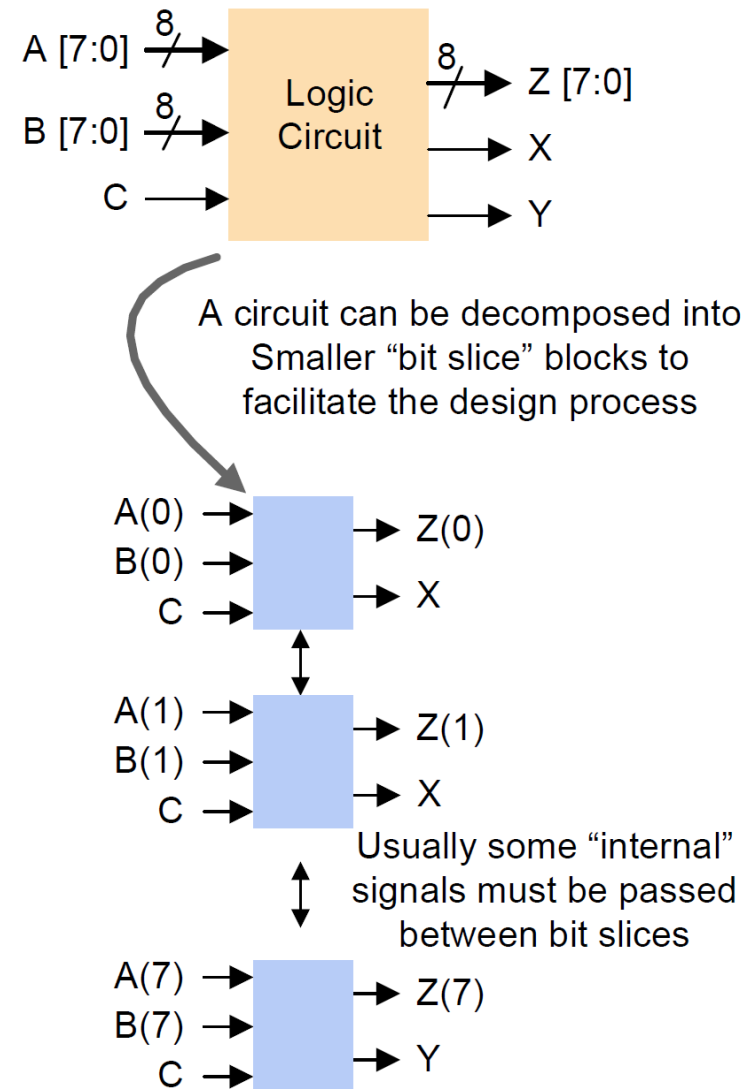- Consider a circuit that works on a pair of bits
- Goal is to create a circuit that can simply be replicated N times
 - once for each bit
 - Some circuits defy this approach
- Information passing between adjacent bits




Comparators

 

```
entity my_comp is  
  port ( A, B : in std_logic_vector (7 downto 0);  
        gt, lt : inout std_logic;  
        eq   : out std_logic);  
end my_comp;
```


```
architecture behavioral of my_comp is  
Begin  
  gt <= '1' when A > B else '0';  
  lt <= '1' when A < B else '0';  
  eq <= not gt and not lt;  
end behavioral;
```

Comparator Bit-Slice Design

 


Operand inputs		Inputs from neighboring slices			Bit-slice outputs		
An	Bn	GTI	LTI	EQI	GTO	LTO	EQO
0	0	1	0	0	1	0	0
0	0	0	1	0	0	1	0
0	0	0	0	1	0	0	1
0	1	φ	φ	φ	0	1	0
1	0	φ	φ	φ	1	0	0
1	1	1	0	0	1	0	0
1	1	0	1	0	0	1	0
1	1	0	0	1	0	0	1


Comparator Bit-Slice Design

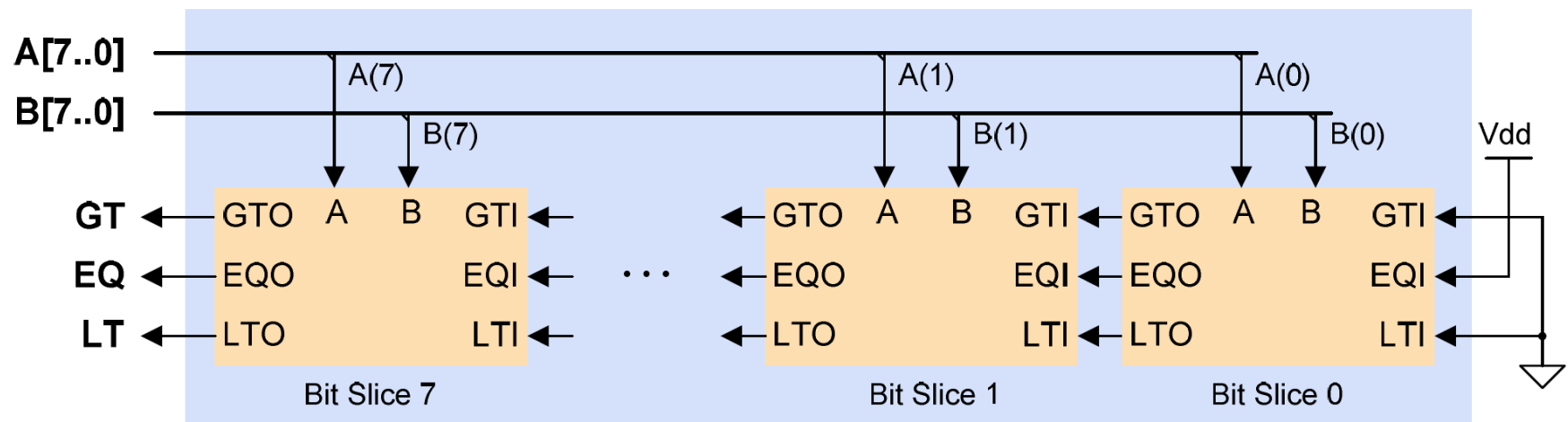


Adders

 


Half Adder

 

Full Adder

 

Arithmetic and Logic Unit (ALU)

 

Op Code	Function
000	A PLUS B
001	A PLUS 1
010	A MINUS B
011	0
100	A XOR B
101	A'
110	A OR B
111	A AND B

8-Bit, 4-Function ALU VHDL

entity ALU **is**

```
port ( A, B : in std_logic_vector (7 downto 0);  
      Sel  : in std_logic_vector (1 downto 0);  
      Y    : out std_logic_vector (7 downto 0));
```

end ALU;

architecture behavioral **of** ALU **is**

Begin

With sel **select**

```
Y <= (A + B) when "00",  
     (A + "00000001") when "01",  
     (A or B) when "10",  
     (A and B) when others;
```

end behavioral;

Assignment

- Lab Project P6
 - Do only on Xilinx Webpack
 - Simulate to show results
 - No Digilent board demo is necessary